

# Introduction to Bandgap Reference Generators

Lecture Notes for  
ELEN 689-602  
by  
Fikret Dülger

# Temperature-Independent References

- Reference voltages and/or currents with little dependence to temperature prove useful in many analog circuits.
- As many process parameters vary with temperature, if a reference is temperature-independent, it is usually process-independent, as well.
- If two quantities with opposite temperature coefficient are added with proper weighting, the resultant quantity theoretically exhibits zero temperature coefficient.

# Temperature-Independent References

- For  $V_1$  and  $V_2$  with opposite temperature dependence, the coefficients  $c_1$  and  $c_2$  can be chosen in such a way that

$$c_1 \frac{\partial V_1}{\partial T} + c_2 \frac{\partial V_2}{\partial T} = 0.$$

Thus, the reference voltage  $V_{ref} = c_1 V_1 + c_2 V_2$  exhibits zero temperature coefficient.

- Among various devices in the semiconductor technology, the characteristics of the bipolar transistors have proven the most reproducible and well-defined quantities that provide positive and negative temperature coefficients.

# Bandgap Voltage Reference

- The most popular technique for both Bipolar and CMOS technologies.
- Generates a fixed dc reference voltage that does not change with temperature.
- Cancels the negative temperature dependence of a PN junction with a positive temperature dependence from a PTAT (proportional-to-absolute-temperature) circuit.


# Bandgap Voltage Reference

- The term with negative temperature dependence is the forward-biased voltage of a diode (usually base-emitter junction).
- The PTAT term is realized by amplifying the voltage difference of two forward-biased diodes ( i.e., base-emitter junctions).


$$V_{ref} = V_{BE} + K . V_{PTAT}$$

- Exact Cancellation of the dependence of  $V_{ref}$  to temperature is not possible because of component tolerances and second order effects such as the nonlinearity of the dependence of  $V_{BE}$  on temperature.

# Bandgap Voltage Reference

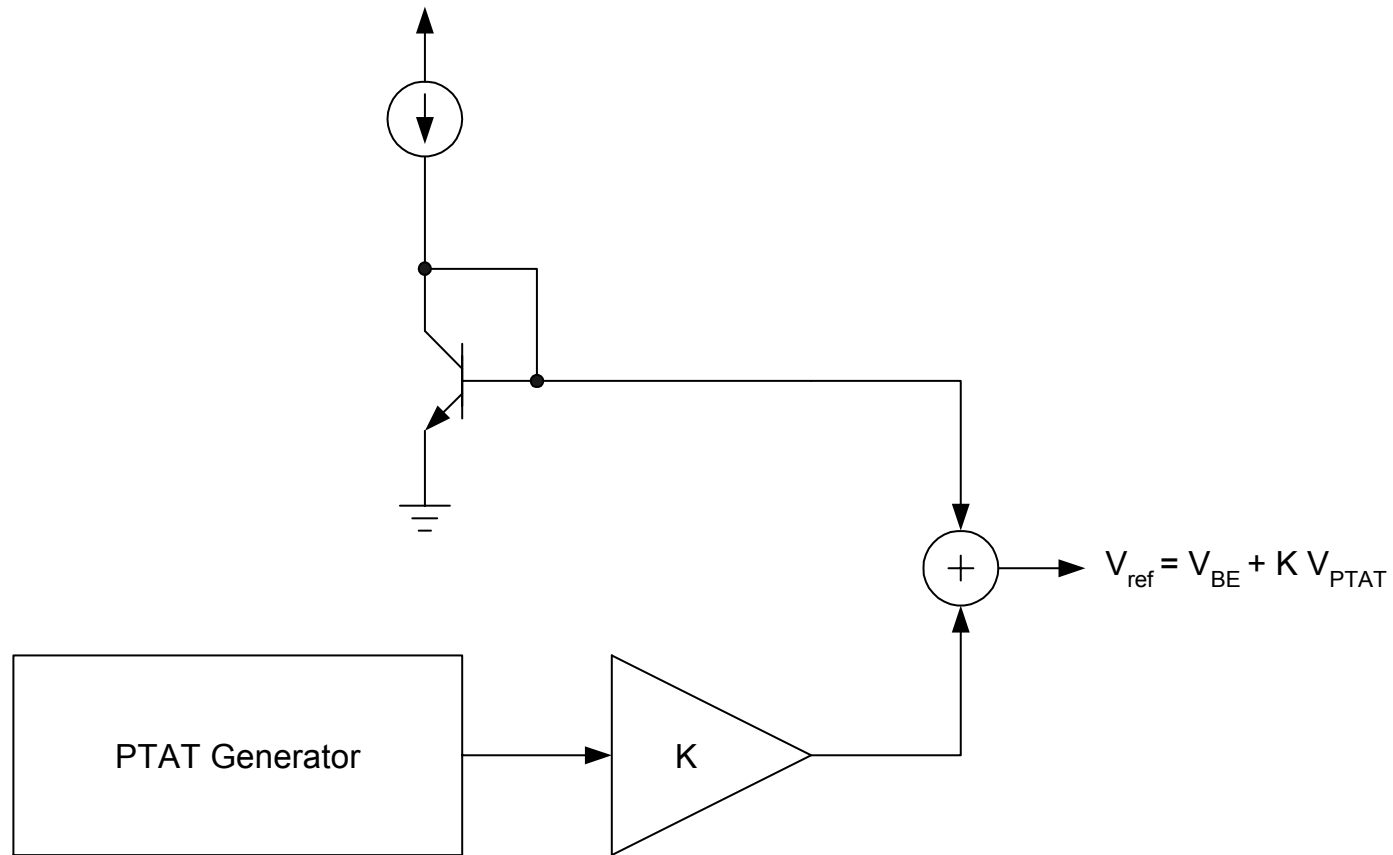


# Bandgap Voltage Reference

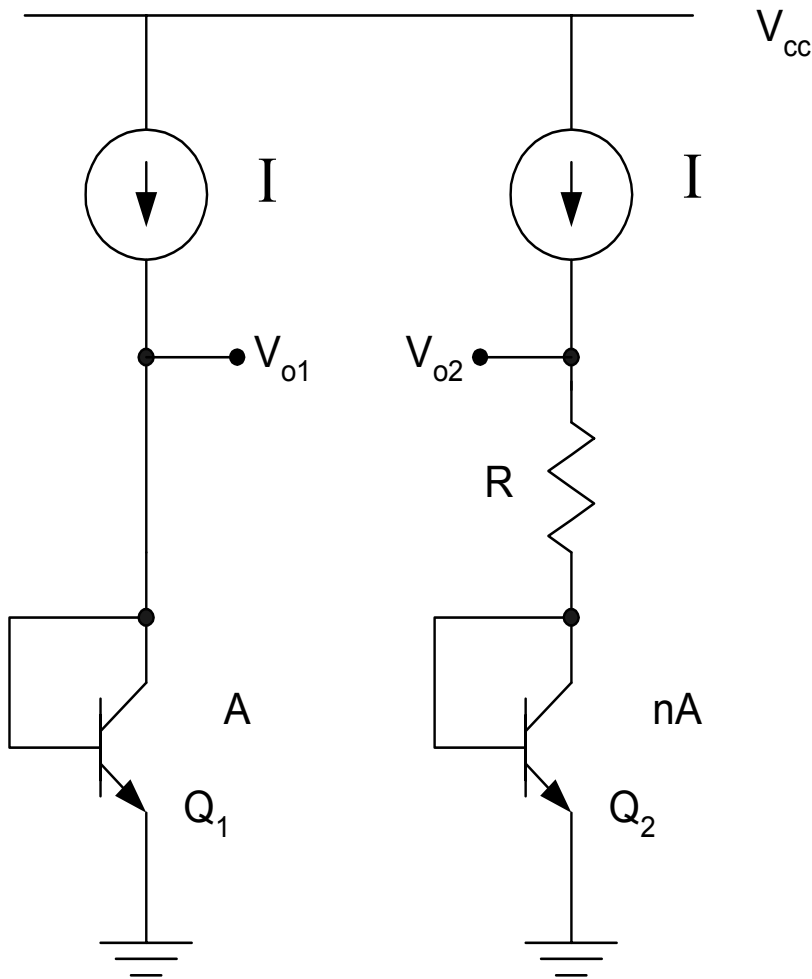

- Conceptual generation of temperature-independent voltage, [3].
- $Q_2$  consists of  $n$  unit transistors in parallel, whereas  $Q_1$  is a unit transistor.
- Somehow forcing  $V_{o1}$  to be equal to  $V_{o2}$ , the voltage drop on  $R$  is determined with the difference of the  $V_{BE}$  voltages of the transistors. This suggests that  $V_{o2}$  can serve as a temperature-independent reference with proper design.

# Bandgap Voltage Reference

## Brokaw's Circuit

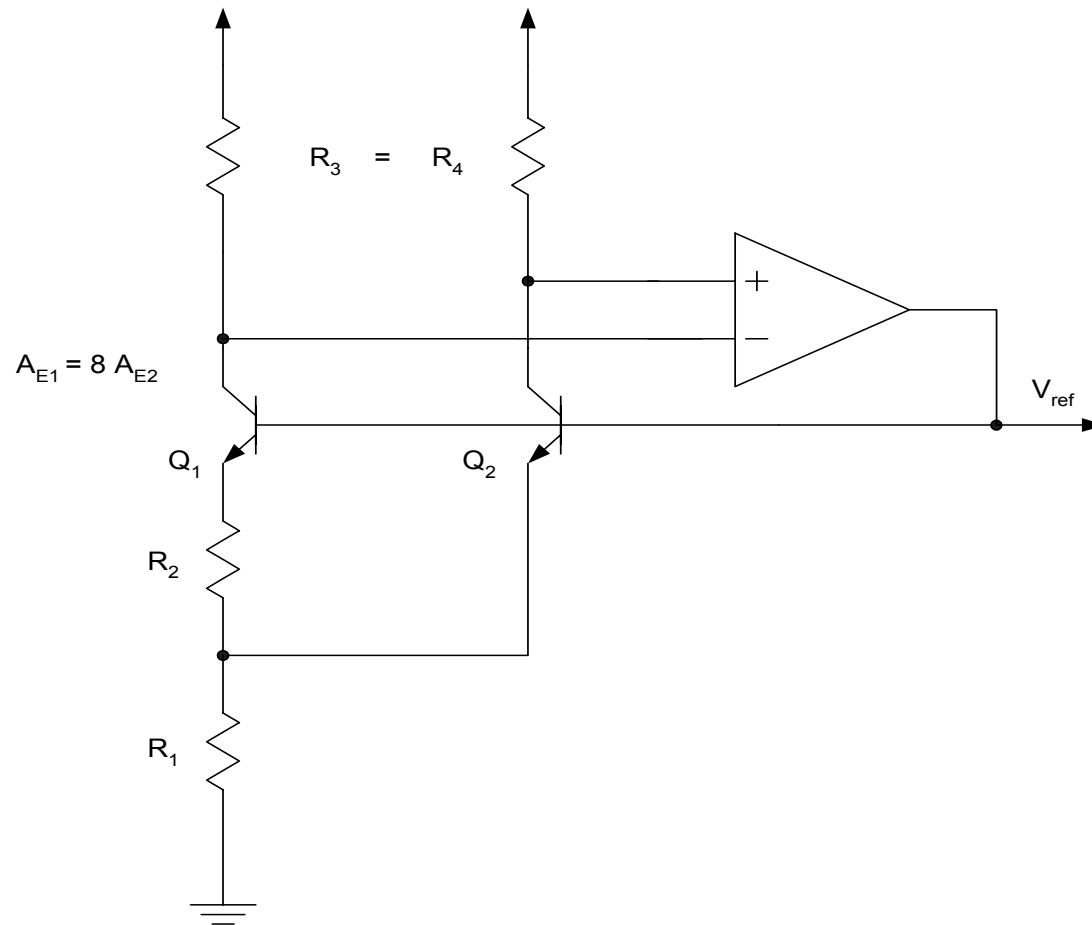



# Bandgap Voltage Reference

- The analysis follows:

$$V_{CQ_1} = V_{CQ_2}, R_3 = R_4, A_{EQ_1} = 8 A_{EQ_2} \Rightarrow \frac{J_{C1}}{J_{C2}} = \frac{1}{8}$$

$$V_{ref} = V_{BE2} + V_{R1}$$

$$V_{R1} = I_{R1} R_1 = 2 I_{R2} R_1 = 2 \frac{V_{R2}}{R_2} R_1$$


$$V_{R2} = V_{BE2} - V_{BE1} = \Delta V_{BE} = V_T \ln \left( \frac{J_{C2}}{J_{C1}} \right)$$

$$\Rightarrow V_{ref} = V_{BE2} + 2 \frac{R_1}{R_2} V_T \ln \left( \frac{J_{C2}}{J_{C1}} \right)$$

# Bandgap Voltage Reference

- In CMOS technologies, where the independent bipolar transistors are not available, parasitic bipolar transistors are used.
- Vertical well transistors are preferred, but lateral transistors (with lower  $\beta_F$ ) can also be used. High base resistance limits the maximum collector currents through the transistors to be less than 0.1mA.
- Realization of PTAT voltage from the difference of the source-gate voltages of two MOS transistors biased in weak inversion is also reported in the literature.

# Hspice Simulations

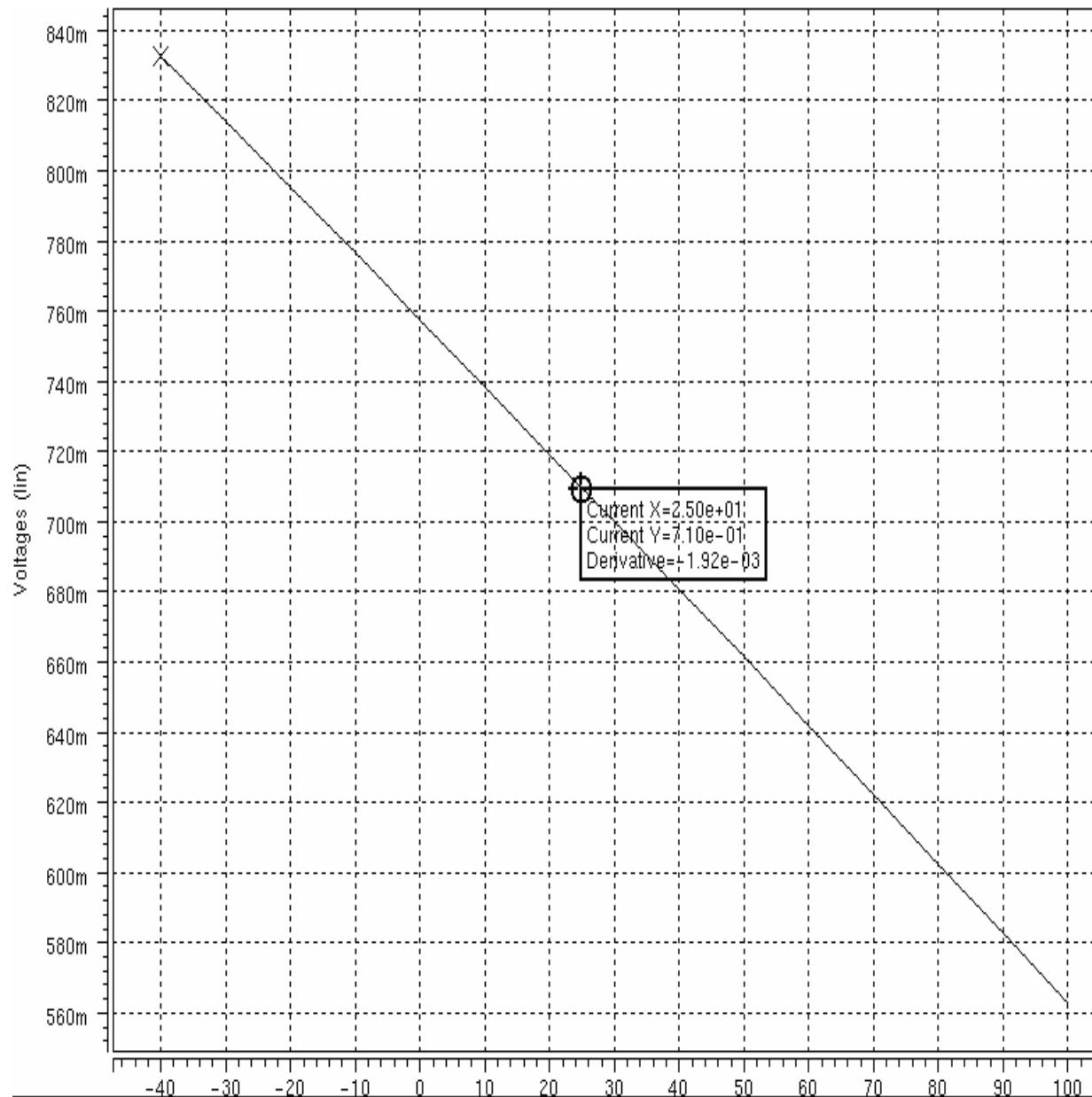

\* HSPICE deck for  $V_{be}$  Temperature  
\* Coefficient at constant  $I_c=100\mu A$

Q1 c c gnd gnd mod

Ic vdd c dc 100e-6

Vdd vdd gnd 2.5

.model mod npn BF=111 VAF=74 EG=1.2058

.option post



.op

\*.dc Ic 10e-6 200e-6 10e-6


.dc sweep temp -40 100 10

.end

# SpectreS Simulations

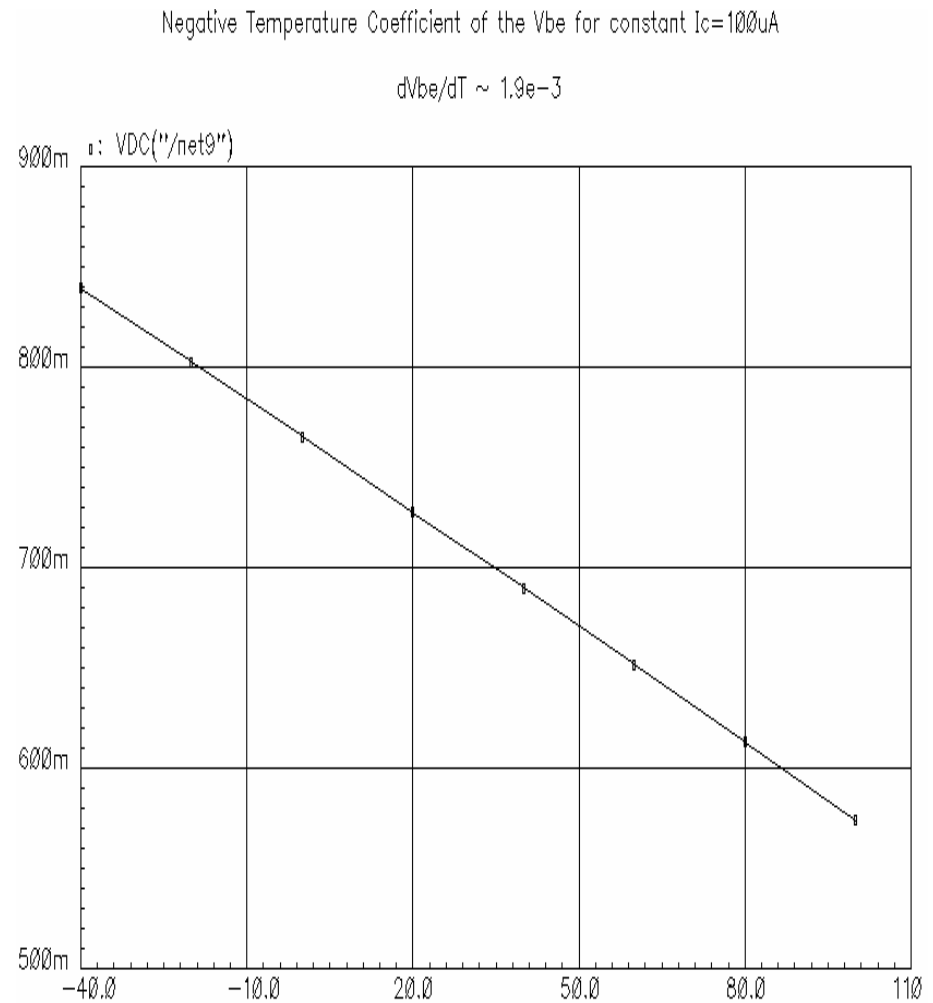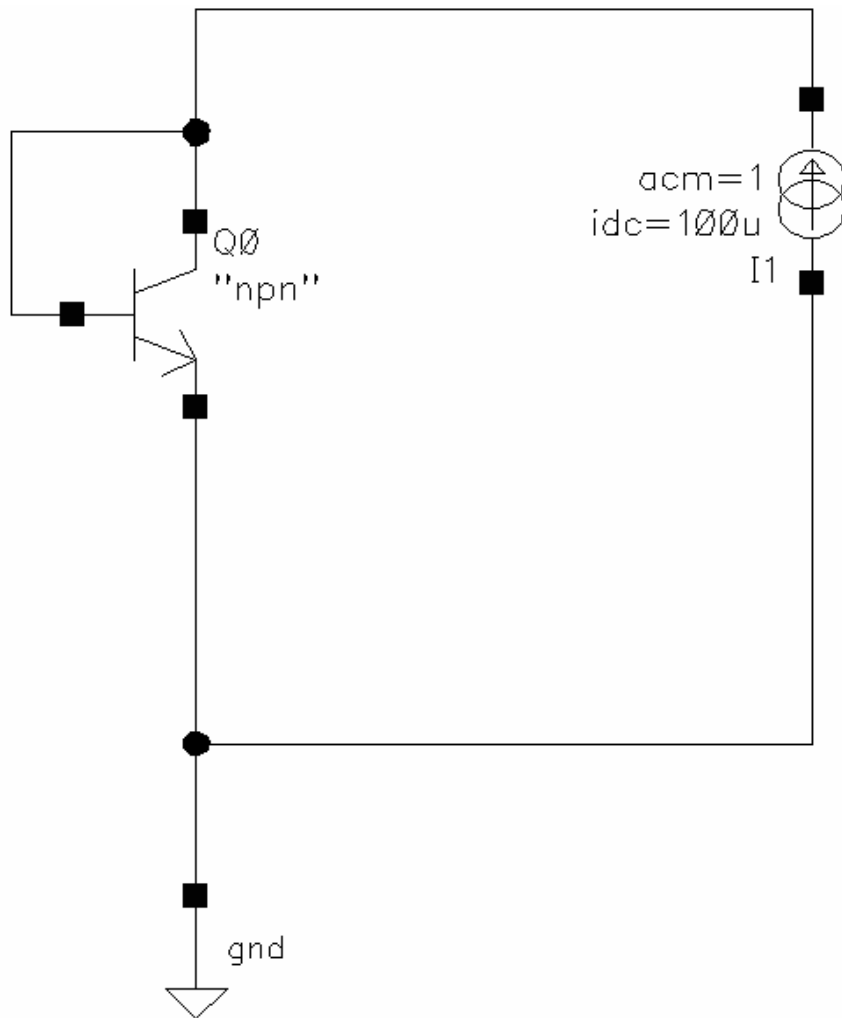


# SpectreS Simulations

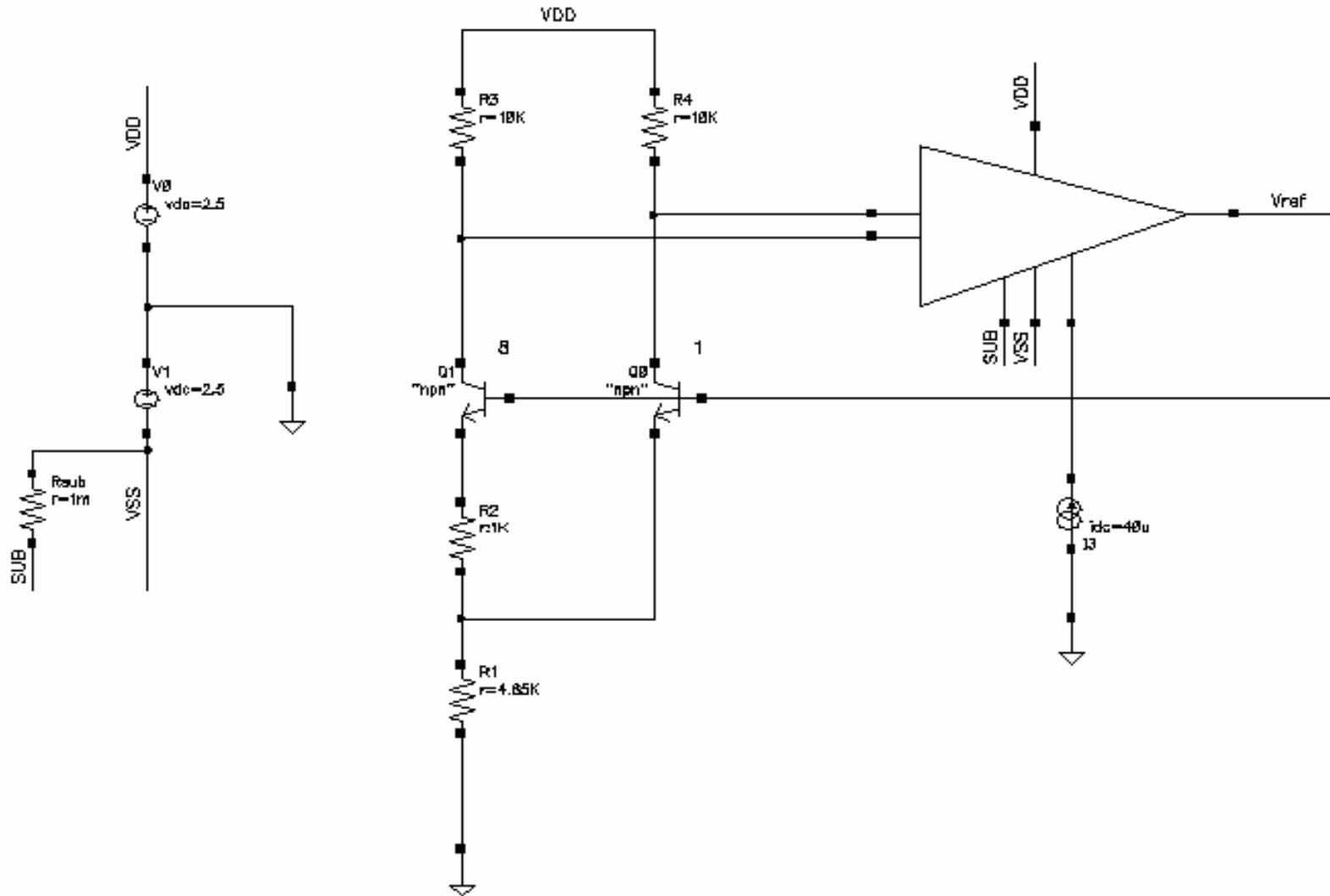
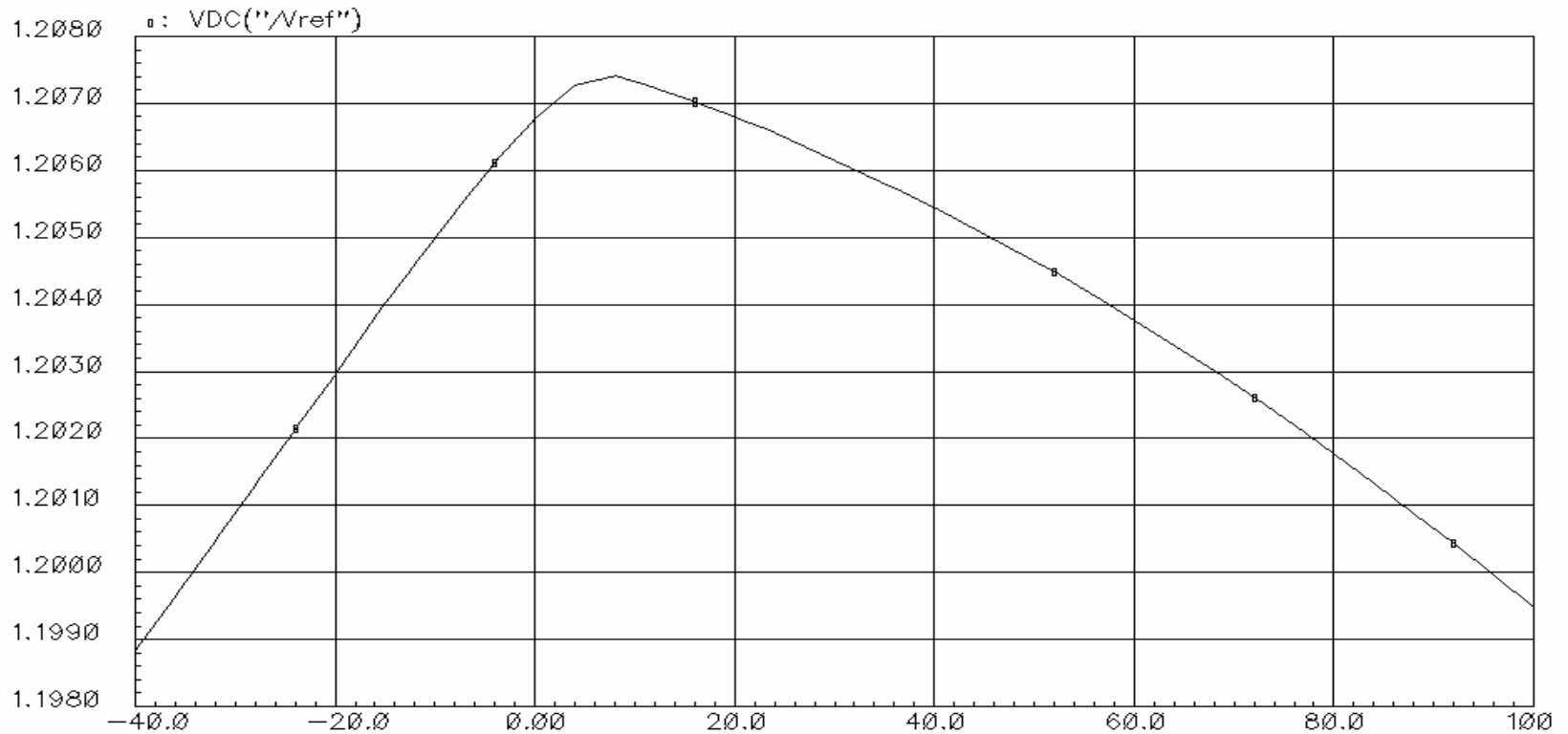
# SpectreS Simulations


Bandgap Reference Voltage  
Temperature Dependence is  $\sim 51\text{ppm}/^\circ\text{C}$


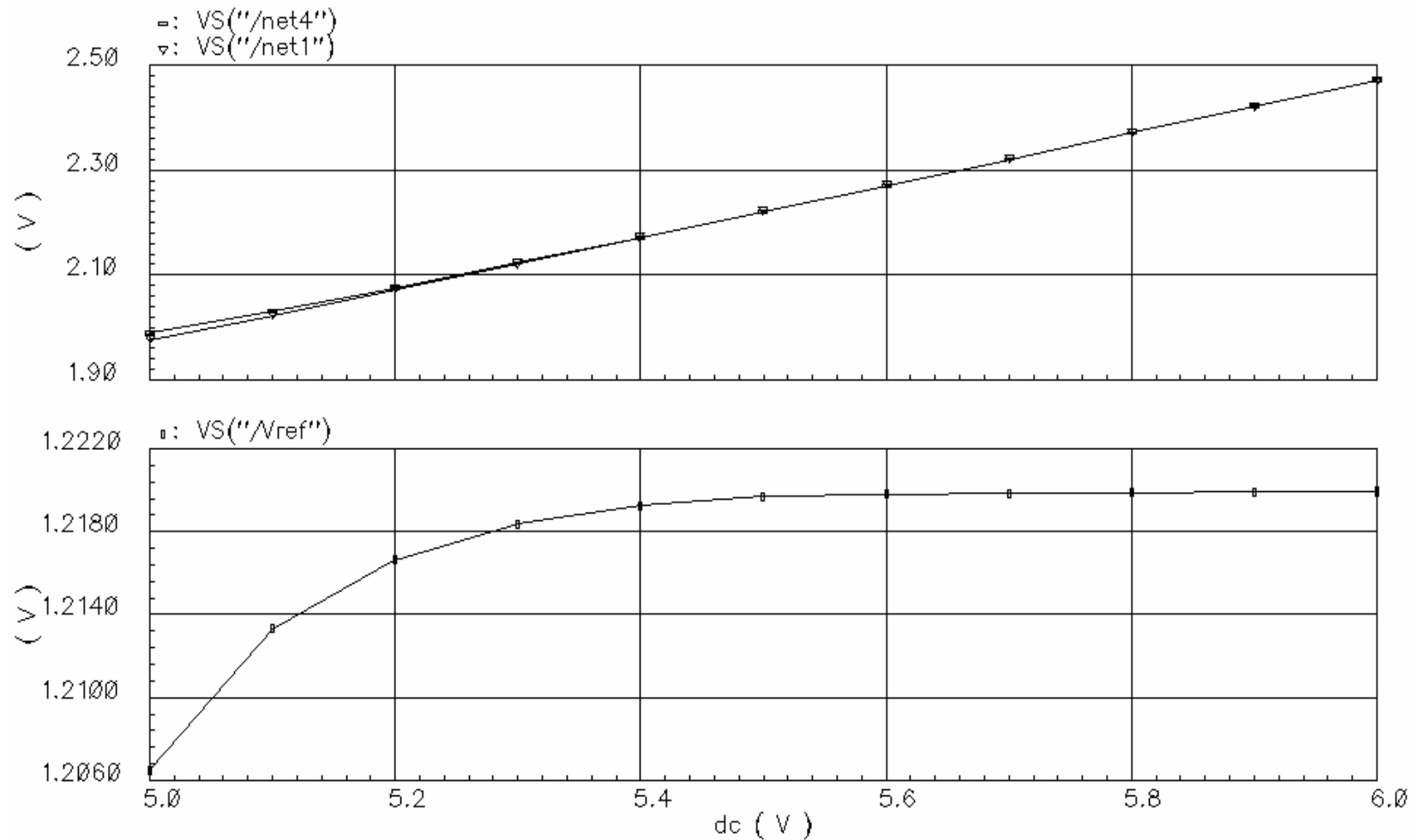
# SpectreS Simulations

Bandgap Reference Voltage

Supply Voltage Dependence is  $\sim 11000\text{ppm/V}$




# Noise Considerations

- Bandgap reference generator introduces noise, as it is the case for all the electronic circuits.
- Noise can be reduced by minimizing the number of components and using small value resistors.
- If MOS devices operating in weak inversion are used, p-channel MOS devices should be preferred due to their lower  $1/f$  noise. Increasing the area of the devices also helps.



# Noise Considerations

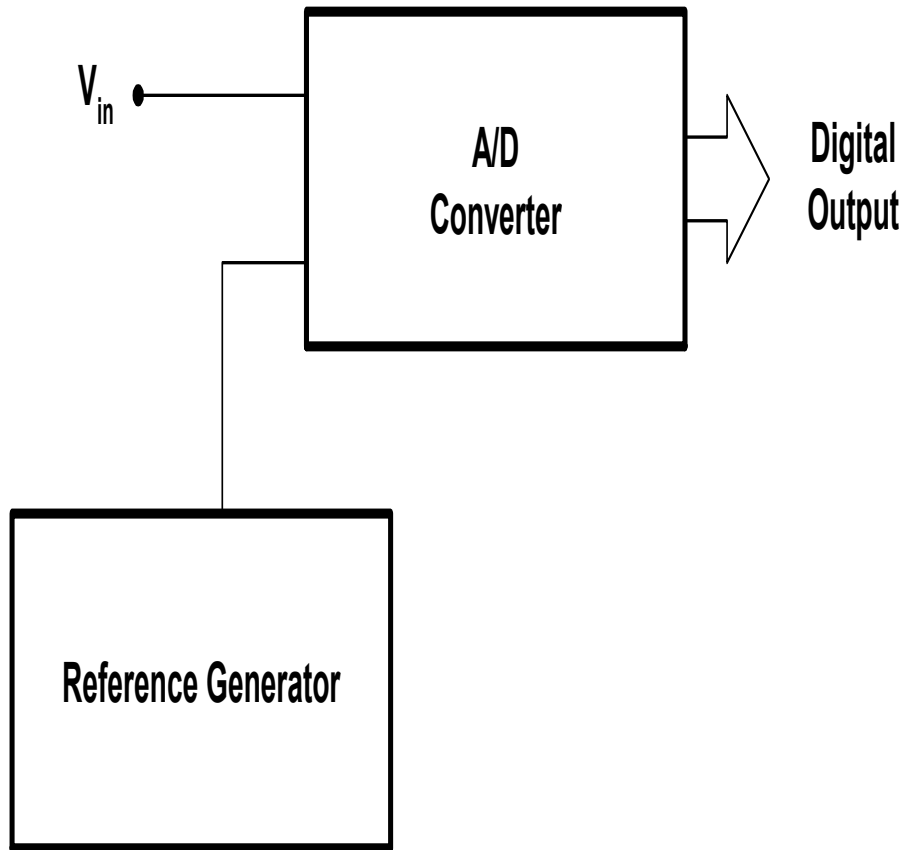

- Conceptual illustration of effect of reference generator noise on the performance of an analog circuit, [3].
- The performance of a high-precision A/D converter, which uses references generated from a bandgap reference to compare its analog input, may considerably be degraded by the output noise of the bandgap reference generator.

# References

- [1] D.A.Johns, K.Martin, Analog Integrated Circuit Design, John Wiley & Sons, Inc., 1997.
- [2] R. L. Geiger, P. E. Allen, N. R. Strader, VLSI Design Techniques for Analog and Digital Circuits, McGraw-Hill, Inc., 1990.
- [3] B.Razavi, Design of Analog CMOS Integrated Circuits, McGraw-Hill, Inc., 2000.
- [4] T.H.Lee, The Design of CMOS Radio-Frequency Integrated Circuits, Cambridge University Press, 1998.